

Spartan6 - DSP48A1

By

Youssef Mohamed Shaban

C Contents

REG & MUX PAIR CODE	2
RTL CODE.....	3
TESTBENCH CODE	4
DO FILE.....	11
RESULT OF THE TESTBENCH.....	12
CONSTRAINT FILE	18
ELABORATION	19
SYNTHESIS.....	20
IMPLEMENTATION	23

Reg & Mux Pair Code

```
reg_mux_pair.v
1  module REG_MUX (IN, CLK, RST, EN, OUT);
2
3  parameter STAGE = 1;
4  parameter WIDTH = 18;
5  parameter RSTTYPE = "SYNC"; //ASYNC
6
7  input CLK, RST, EN;
8  input [WIDTH - 1 : 0] IN;
9  output reg [WIDTH - 1 : 0] OUT;
10
11 generate
12     if (STAGE == 1 && RSTTYPE == "ASYNC") begin
13         always @(posedge CLK or posedge RST) begin
14             if (RST)
15                 OUT <= 0;
16
17             else if (EN)
18                 OUT <= IN;
19         end
20     end
21
22     else if (STAGE == 1 && RSTTYPE == "SYNC") begin
23         always @(posedge CLK) begin
24             if (RST)
25                 OUT <= 0;
26
27             else if (EN)
28                 OUT <= IN;
29         end
30     end
31
32     else if (~STAGE) begin
33         always @(*) begin
34             OUT = IN;
35         end
36     end
37
38 endgenerate
39 endmodule
```

RTL Code

```

DSPv
1  //----- DSP48A1 -----//
2
3  module DSP_48A1 (A,B,C,D,CLK,CARRYIN,RSTCARRYIN,RSTOPMODE,RSTA,RSTB,RSTC,RSTD,RSTM,RSTP,
4  |               CEA,CEB,CEM,CEP,CEC,CED,CECARRYIN,CEOPMODE,PCIN,OPMODE,BCIN,
5  |               Bcout,PCout,P,M,CARRYOUT,CARRYOUTF);
6
7  parameter A0REG = 0;
8  parameter A1REG = 1;
9  parameter B0REG = 0;
10 parameter B1REG = 1;
11
12 parameter CREG = 1;
13 parameter DREG = 1;
14 parameter MREG = 1;
15 parameter PREG = 1;
16 parameter CARRYINREG = 1;
17 parameter CARRYOUTREG = 1;
18 parameter OPMODEREG = 1;
19
20 parameter CARRYINSEL = "OPMODES"; //CARRYIN
21 parameter B_INPUT = "DIRECT"; //CASCADE
22 parameter RSTTYPE = "SYNC"; //ASYNC
23
24 input CLK, CARRYIN;
25 input RSTCARRYIN, RSTOPMODE, RSTA, RSTB, RSTC, RSTD, RSTM, RSTP;
26 input CEA, CEB, CEM, CEP, CEC, CED, CECARRYIN, CEOPMODE;
27 input [17:0] A, B, D;
28 input [47:0] C, PCIN;
29 input [7:0] OPMODE;
30 input [17:0] BCIN;
31
32 output CARRYOUT, CARRYOUTF;
33 output [17:0] Bcout;
34 output [35:0] M;
35 output [47:0] PCout, P;
36
37 //-----//
38
39 wire [7:0] opmode_r;
40 wire [17:0] a0_out, b0_out, d_out, b_in, pre_adder_out, bypass_b;
41 wire [47:0] c_out;
42
43 REG_MUX #(.STAGE(OPMODEREG), .WIDTH(8), .RSTTYPE(RSTTYPE)) OPMODE_REG (OPMODE, CLK, RSTOPMODE, CEOPMODE, opmode_r);
44 REG_MUX #(.STAGE(A0REG), .WIDTH(18), .RSTTYPE(RSTTYPE)) A0_REG (A, CLK, RSTA, CEA, a0_out);
45 REG_MUX #(.STAGE(B0REG), .WIDTH(18), .RSTTYPE(RSTTYPE)) B0_REG (b_in, CLK, RSTB, CEB, b0_out);
46 REG_MUX #(.STAGE(CREG), .WIDTH(48), .RSTTYPE(RSTTYPE)) C_REG (C, CLK, RSTC, CEC, c_out);
47 REG_MUX #(.STAGE(DREG), .WIDTH(18), .RSTTYPE(RSTTYPE)) D_REG (D, CLK, RSTD, CED, d_out);
48
49 assign b_in = (B_INPUT == "DIRECT")? B : (B_INPUT == "CASCADE")? BCIN : 18'b0;
50 assign pre_adder_out = (opmode_r[6])? (d_out - b0_out) : (d_out + b0_out);
51 assign bypass_b = (opmode_r[4])? pre_adder_out : b0_out;
52
53 //-----//
54
55 wire [17:0] a1_out, b1_out;
56 wire [35:0] multiplier_out, m_out;
57
58 reg [47:0] x_out, z_out;
59
60 REG_MUX #(.STAGE(A1REG), .WIDTH(18), .RSTTYPE(RSTTYPE)) A1_REG (a0_out, CLK, RSTA, CEA, a1_out);
61 REG_MUX #(.STAGE(B1REG), .WIDTH(18), .RSTTYPE(RSTTYPE)) B1_REG (bypass_b, CLK, RSTB, CEB, b1_out);
62 REG_MUX #(.STAGE(MREG), .WIDTH(36), .RSTTYPE(RSTTYPE)) M_REG (multiplier_out, CLK, RSTM, CEM, m_out);
63
64 assign multiplier_out = a1_out * b1_out;
65
```

```

66 //----- X_MUX & Z_MUX -----//
67 always @(*) begin
68     case (opmode_r[1:0])
69         0 : x_out = 0;
70         1 : x_out = { {12{m_out[35]}} , m_out};
71         2 : x_out = P;
72         3 : x_out = {d_out[11:0] , a1_out , b1_out};
73     endcase
74
75     case (opmode_r[3:2])
76         0 : z_out = 0;
77         1 : z_out = PCIN;
78         2 : z_out = P;
79         3 : z_out = c_out;
80     endcase
81 end
82
83 //-----//
84
85 wire carry_cascade_out , COUT , CIN;
86 wire [47:0] post_adder_out;
87
88 REG_MUX #(.STAGE(PREG) , .WIDTH(48) , .RSTTYPE(RSTTYPE)) P_REG (post_adder_out , CLK , RSTP , CEP , P);
89 REG_MUX #(.STAGE(CARRYINREG) , .WIDTH(1) , .RSTTYPE(RSTTYPE)) CVI_REG (carry_cascade_out , CLK , RSTCARRYIN , CECARRYIN , CIN);
90 REG_MUX #(.STAGE(CARRYOUTREG) , .WIDTH(1) , .RSTTYPE(RSTTYPE)) CYO_REG (COUT , CLK , RSTCARRYIN , CECARRYIN , CARRYOUT);
91
92 assign carry_cascade_out = (CARRYINSEL == "OPMODES")? opmode_r[5] : (B_INPUT == "CARRYIN")? CARRYIN : 1'b0;
93 assign {COUT , post_adder_out} = (opmode_r[7])? (z_out - (x_out + CIN)) : (z_out + x_out + CIN);
94 assign CARRYOUTF = CARRYOUT;
95 assign PCOUT = P;
96 assign BCOUT = b1_out;
97 assign M = ~(~m_out); //buf( M , m_out);
98
99 endmodule

```

Testbench Code

- This test bench is:
 - A mix between directed and randomized test benches
 - Self-checking test bench
- **Note:**
 The explanation of the testbench code and the reasons for each input pattern in each test case is in the “**Result of the Testbench**” section (Page 12)

```

//----- DSP Testbench -----//

module TB_DSP ();

parameter A0REG = 1;//
parameter A1REG = 1;
parameter B0REG = 1;//
parameter B1REG = 1;

```

```

parameter CREG = 1;
parameter DREG = 1;
parameter MREG = 1;
parameter PREG = 1;
parameter CARRYINREG = 1;
parameter CARRYOUTREG = 1;
parameter OPMODEREG = 1;

parameter CARRYINSEL = "OPMODE5"; //CARRYIN
parameter B_INPUT = "DIRECT"; //CASCADE
parameter RSTTYPE = "SYNC"; //ASYNC

reg clk, CARRYIN;
reg RSTCARRYIN, RSTOPMODE, RSTA, RSTB, RSTC, RSTD, RSTM, RSTP;
reg CEA, CEB, CEM, CEP, CEC, CED, CECARRYIN, CEOPMODE;
reg [17:0] A, B, D, PRE_EXP;
reg [47:0] C, PCIN;
reg [7:0] OPMODE;
reg [17:0] BCIN;

wire CARRYOUT , CARRYOUTF;
wire [17:0] BCOUT;
wire [35:0] M;
wire [47:0] PCOUT , P;

reg [47:0] EXPECTED;

DSP48A1
#(A0REG,A1REG,B0REG,B1REG,CREG,DREG,MREG,PREG,CARRYINREG,CARRYOUTREG,OPMODEREG,CARRYINSEL,B_INPUT,RSTTYPE)
    DUT
(A,B,C,D,clk,CARRYIN,RSTCARRYIN,RSTOPMODE,RSTA,RSTB,RSTC,RSTD,RSTM,RSTP,
    CEA, CEB, CEM, CEP, CEC, CED, CECARRYIN, CEOPMODE, PCIN, OPMODE,
BCIN,
    BCOUT, PCOUT, P, M, CARRYOUT, CARRYOUTF);

initial begin
    clk = 0;
    forever
        #10 clk = ~clk;
end

initial begin
    $display("\n-----> Testing Reset <-----\n");

```

```

RSTOPMODE= 1; RSTA= 1; RSTB= 1; RSTC= 1; RSTD= 1; RSTM= 1; RSTP= 1; RSTM= 1;
RSTCARRYIN= 1;

repeat (10) begin
    CEA=$random; CEB=$random; CEM=$random;
    CEP=$random; CEC=$random; CED=$random;
    CECARRYIN=$random; CEOPMODE=$random; CARRYIN=$random;
    OPMODE=$random; PCIN=$random; BCIN=$random;
    A=$random; B=$random; C=$random; D=$random;

    EXPECTED = 0;

    @(negedge clk);

    if (P != EXPECTED) begin
        $display("ERROR!! Incorrect Output :(");
        $stop;
    end
end

//-----enable-----
    $display("\n-----> Testing Enable <-----\n");

RSTOPMODE= 0; RSTA= 0; RSTB= 0; RSTC= 0; RSTD= 0; RSTM= 0; RSTP= 0; RSTM= 0;
RSTCARRYIN= 0;
CEA= 0; CEB= 0; CEM= 0; CEP= 0; CEC= 0; CED= 0; CECARRYIN= 0; CEOPMODE= 0;

repeat (10) begin
    CARRYIN=$random;
    OPMODE=$random; PCIN=$random; BCIN=$random;
    A=$random; B=5; C=$random; D=$random;

    EXPECTED = 0;

    @(negedge clk);

    if (P != EXPECTED) begin
        $display("ERROR!! Incorrect Output :(");
        $stop;
    end
end

//-----bypass B-----
    $display("\n-----> Testing bypass B <-----\n");

```

```

CEA= 1; CEB= 1; CEM= 1; CEP= 1; CEC= 1; CED= 1; CECARRYIN= 1; CEOPMODE= 1;

// OPMODE = 8'b 7_6_5_4_32_10;
OPMODE = 8'b 0_0_0_0_11_01;

A = 1; C = 0;

repeat (10) begin

    B = $urandom_range(0,15);

    PCIN=$random; BCIN=$random; D=$random;

    EXPECTED = B;

    repeat (4) @(negedge clk);

    if (P != EXPECTED) begin
        $display("ERROR!! Incorrect Output :(");
        $stop;
    end
end

//-----operation-----
$display("\n-----> Testing arithmetic
operations <-----\n");

RSTOPMODE= 1; RSTA= 1; RSTB= 1; RSTC= 1; RSTD= 1; RSTM= 1; RSTP= 1; RSTM= 1;
RSTCARRYIN= 1;

repeat (4) @(negedge clk);

RSTOPMODE= 0; RSTA= 0; RSTB= 0; RSTC= 0; RSTD= 0; RSTM= 0; RSTP= 0; RSTM= 0;
RSTCARRYIN= 0;

OPMODE[4:0] = 5'b 1_11_01;

repeat (100) begin

    D = $urandom_range(7);
    B = $urandom_range(7);
    A = $urandom_range(7);
    C = $urandom_range(7);
    OPMODE[7:5] = $random;

```

```

        case (OPMODE[7:6])
            2'b00 : begin PRE_EXP = D+B; EXPECTED = C + (A*PRE_EXP + OPMODE[5]);
end
            2'b01 : begin PRE_EXP = D-B; EXPECTED = C + (A*PRE_EXP + OPMODE[5]);
end
            2'b10 : begin PRE_EXP = D+B; EXPECTED = C - (A*PRE_EXP + OPMODE[5]);
end
            2'b11 : begin PRE_EXP = D-B; EXPECTED = C - (A*PRE_EXP + OPMODE[5]);
end

        endcase

        repeat (4) @(negedge clk);

        if (P != EXPECTED) begin
            $display("ERROR!! Incorrect Output :(");
            $stop;
        end
    end

//-----accumulator x -----
    $display("\n-----> Testing Accumulator
through X <-----\n");

    RSTOPMODE= 1; RSTA= 1; RSTB= 1; RSTC= 1; RSTD= 1; RSTM= 1; RSTP= 1; RSTM= 1;
RSTCARRYIN= 1;
    @(negedge clk);
    RSTOPMODE= 0; RSTA= 0; RSTB= 0; RSTC= 0; RSTD= 0; RSTM= 0; RSTP= 0; RSTM= 0;
RSTCARRYIN= 0;

    OPMODE = 8'b 0_0_0_0_11_10;
    C = 2;
    EXPECTED = 2;

    repeat (2) @(negedge clk);

    repeat (100) begin

        D = $random;
        B = $random;
        A = $random;

        EXPECTED = EXPECTED + 2;

        @(negedge clk);

```



```

        if (P != EXPECTED) begin
            $display("ERROR!! Incorrect Output :(");
            $stop;
        end
    end

    //-----accumulator z-----
    $display("\n-----> Testing Accumlator
through Z <-----\n");

    RSTOPMODE= 1; RSTA= 1; RSTB= 1; RSTC= 1; RSTD= 1; RSTM= 1; RSTP= 1; RSTM= 1;
RSTCARRYIN= 1;
    @(negedge clk);
    RSTOPMODE= 0; RSTA= 0; RSTB= 0; RSTC= 0; RSTD= 0; RSTM= 0; RSTP= 0; RSTM= 0;
RSTCARRYIN= 0;

    OPMODE = 8'b 0_0_0_0_10_01;
    B = 2;
    A = 1;

    EXPECTED = 2;

    repeat (4) @(negedge clk);

    repeat (100) begin
        D = $random;
        C = $random;

        EXPECTED = EXPECTED + 2;

        @(negedge clk);

        if (P != EXPECTED) begin
            $display("ERROR!! Incorrect Output :(");
            $stop;
        end
    end

    //-----mux 0-----
    $display("\n-----> Testing Placing all
zeros <-----\n");

    OPMODE[7:0] = 8'b 0_0_0_0_00_00;
    repeat (10) begin

        D = $random;
        B = $random;

```

```

    A = $random;
    C = $random;

    EXPECTED = 0;
    repeat (2) @(negedge clk);

    if (P != EXPECTED) begin
        $display("ERROR!! Incorrect Output :(");
        $stop;
    end
end

//-----conc & pcin-----
    $display("\n-----> Testing
Concatenation & PCIN <-----\n");

    OPMODE[7:0] = 8'b 0_0_0_0_01_11;
    repeat (100) begin
        PCIN = $random;
        D = $random;
        B = $random;
        A = $random;
        C = $random;

        EXPECTED = PCIN + {D[11:0] , A , B};
        repeat (4) @(negedge clk);

        if (P != EXPECTED) begin
            $display("ERROR!! Incorrect Output :(");
            $stop;
        end
    end

    //If the simulation reached this line then no errors were found
    $display("\n---> NO ERRORS, All Outputs are Correct :) <---\n");
    $stop;
end

initial begin
    $monitor("CLK= %b ,D= %d ,B= %d ,A= %d ,C= %d ,OPMODE= %b_%b_%b ,BCOUT= %d
,M= %d ,CARRYOUT= %b ,P= %d ,EXPECTED = %d",
            clk , D, B, A, C, OPMODE[7:6], OPMODE[5], OPMODE[4:0], BCOUT, M,
            CARRYOUT, P, EXPECTED);
end

endmodule

```


DO File

```
2.do
1  .main clear
2
3  vlib work
4
5  vlog DSP.v TB_DSP.v reg_mux_pair.v
6
7  vsim -voptargs=+acc work.TB_DSP
8
9  #add wave *
10
11 add wave -radix decimal -position insertpoint \
12 sim:/TB_DSP/CARRYIN \
13 sim:/TB_DSP/RSTCARRYIN \
14 sim:/TB_DSP/RSTOPMODE \
15 sim:/TB_DSP/RSTA \
16 sim:/TB_DSP/RSTB \
17 sim:/TB_DSP/RSTC \
18 sim:/TB_DSP/RSTD \
19 sim:/TB_DSP/RSTM \
20 sim:/TB_DSP/RSTP \
21 sim:/TB_DSP/CEA \
22 sim:/TB_DSP/CEB \
23 sim:/TB_DSP/CEM \
24 sim:/TB_DSP/CEP \
25 sim:/TB_DSP/CEC \
26 sim:/TB_DSP/CED \
27 sim:/TB_DSP/CECARRYIN \
28 sim:/TB_DSP/CEOPMODE \
29 sim:/TB_DSP/PCIN \
30 sim:/TB_DSP/BCIN \
31 sim:/TB_DSP/OPMODE \
32 sim:/TB_DSP/C \
33 sim:/TB_DSP/B \
34 sim:/TB_DSP/D \
35 sim:/TB_DSP/A \
36 {sim:/TB_DSP/OPMODE[5]}
37
38 add wave -color magenta -position insertpoint \
39 sim:/TB_DSP/clk
```

```
2.do
40
41 add wave -radix decimal -color red -position insertpoint \
42 sim:/TB_DSP/EXPECTED
43
44 add wave -radix decimal -color cyan -position insertpoint \
45 sim:/TB_DSP/P \
46 sim:/TB_DSP/CARRYOUT \
47 sim:/TB_DSP/CARRYOUTF \
48 sim:/TB_DSP/BCOUT \
49 sim:/TB_DSP/M \
50 sim:/TB_DSP/PCOUT
51
52
53 add wave -radix decimal -color orange -position insertpoint \
54 sim:/TB_DSP/DUT/opmode_r \
55 sim:/TB_DSP/DUT/a0_out \
56 sim:/TB_DSP/DUT/b0_out \
57 sim:/TB_DSP/DUT/d_out \
58 sim:/TB_DSP/DUT/b_in \
59 sim:/TB_DSP/DUT/pre_adder_out \
60 sim:/TB_DSP/DUT/bypass_b \
61 sim:/TB_DSP/DUT/c_out \
62 sim:/TB_DSP/DUT/a1_out \
63 sim:/TB_DSP/DUT/b1_out \
64 sim:/TB_DSP/DUT/multiplier_out \
65 sim:/TB_DSP/DUT/m_out \
66 sim:/TB_DSP/DUT/x_out \
67 sim:/TB_DSP/DUT/z_out \
68 sim:/TB_DSP/DUT/carry_cascade_out \
69 sim:/TB_DSP/DUT/COUT \
70 sim:/TB_DSP/DUT/CIN \
71 sim:/TB_DSP/DUT/post_adder_out
72
73 run -all
74
75 #quit -sim
76
```

Result of the Testbench

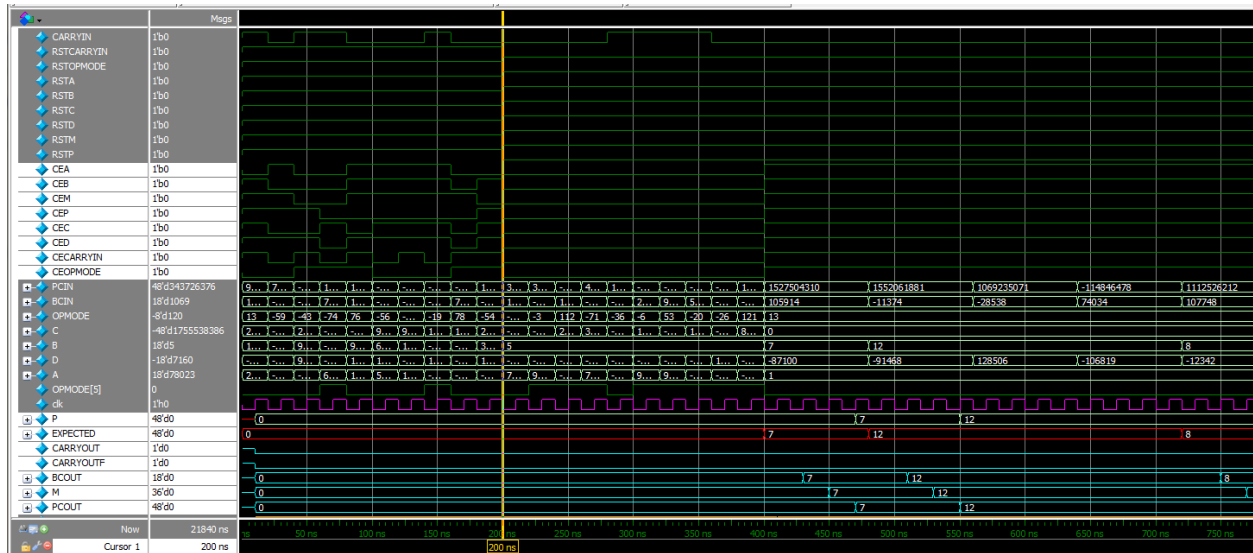
- Testing reset and enable signals of all registers



```
# -----> Testing Reset <-----
# CLK= 0 ,A= 206022 ,B= 128908 ,C= 22509 ,D= 2097015289 ,OPMODE= 00_0_01101 BCOUT= x ,M= x ,CARRYOUT= x ,P= x ,EXPECTED = 0
# CLK= 1 ,A= 206022 ,B= 128908 ,C= 22509 ,D= 2097015289 ,OPMODE= 00_0_01101 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 231178 ,B= 206437 ,C= 219181 ,D= 281473666998883 ,OPMODE= 11_0_00101 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 231178 ,B= 206437 ,C= 219181 ,D= 281473666998883 ,OPMODE= 11_0_00101 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 91402 ,B= 94927 ,C= 256285 ,D= 293882147 ,OPMODE= 11_0_10101 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 91402 ,B= 94927 ,C= 256285 ,D= 293882147 ,OPMODE= 11_0_10101 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 245361 ,B= 253226 ,C= 66236 ,D= 281472927242763 ,OPMODE= 10_1_10110 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 245361 ,B= 253226 ,C= 66236 ,D= 281472927242763 ,OPMODE= 10_1_10110 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 103516 ,B= 90295 ,C= 109048 ,D= 281474167494303 ,OPMODE= 01_0_01100 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 103516 ,B= 90295 ,C= 109048 ,D= 281474167494303 ,OPMODE= 01_0_01100 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 124729 ,B= 65662 ,C= 56082 ,D= 921010541 ,OPMODE= 11_0_01000 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 124729 ,B= 65662 ,C= 56082 ,D= 921010541 ,OPMODE= 11_0_01000 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 242851 ,B= 113702 ,C= 104954 ,D= 966137715 ,OPMODE= 10_0_00110 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 242851 ,B= 113702 ,C= 104954 ,D= 966137715 ,OPMODE= 10_0_00110 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 130884 ,B= 169183 ,C= 189109 ,D= 1022433657 ,OPMODE= 11_1_01101 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 130884 ,B= 169183 ,C= 189109 ,D= 1022433657 ,OPMODE= 11_1_01101 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 246968 ,B= 166456 ,C= 244150 ,D= 1020364665 ,OPMODE= 01_0_01110 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 246968 ,B= 166456 ,C= 244150 ,D= 1020364665 ,OPMODE= 01_0_01110 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 1897 ,B= 39684 ,C= 203334 ,D= 2077385207 ,OPMODE= 11_0_01010 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 1897 ,B= 39684 ,C= 203334 ,D= 2077385207 ,OPMODE= 11_0_01010 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
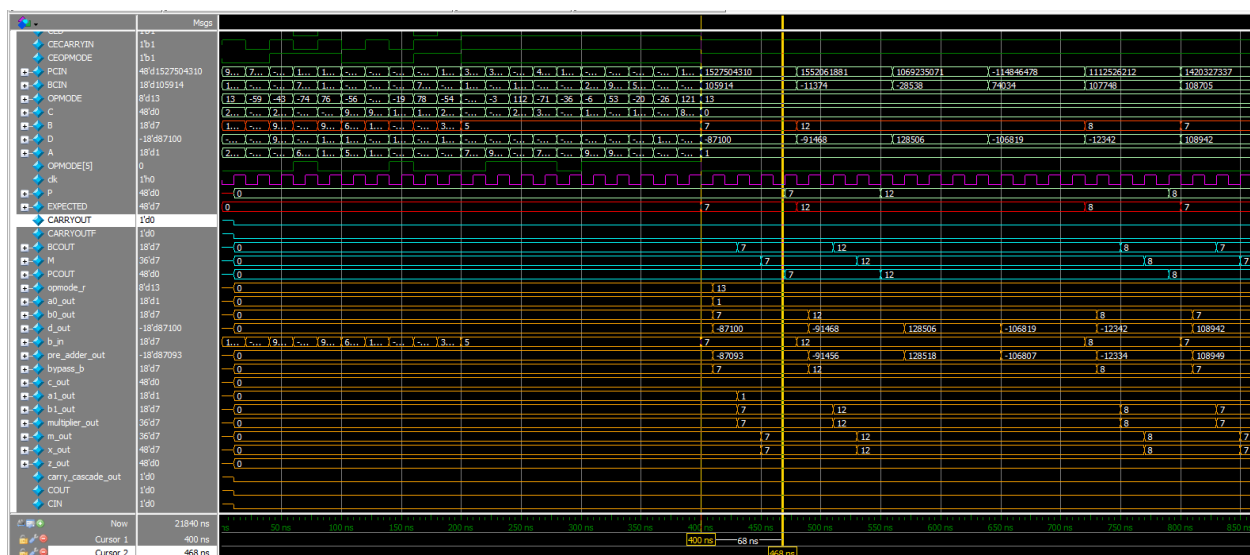
# -----> Testing Enable <-----
# CLK= 0 ,A= 254984 ,B= 5 ,C= 78023 ,D= 281473221172270 ,OPMODE= 10_0_01000 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 254984 ,B= 5 ,C= 78023 ,D= 281473221172270 ,OPMODE= 10_0_01000 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 247357 ,B= 5 ,C= 92038 ,D= 281474661353690 ,OPMODE= 11_1_11101 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 247357 ,B= 5 ,C= 92038 ,D= 281474661353690 ,OPMODE= 11_1_11101 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 132565 ,B= 5 ,C= 176990 ,D= 2101836282 ,OPMODE= 01_1_10000 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 132565 ,B= 5 ,C= 176990 ,D= 2101836282 ,OPMODE= 01_1_10000 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 137910 ,B= 5 ,C= 74176 ,D= 321232678 ,OPMODE= 10_1_11001 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 137910 ,B= 5 ,C= 74176 ,D= 321232678 ,OPMODE= 10_1_11001 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 243407 ,B= 5 ,C= 170878 ,D= 281474667217115 ,OPMODE= 11_0_11100 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 243407 ,B= 5 ,C= 170878 ,D= 281474667217115 ,OPMODE= 11_0_11100 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 235088 ,B= 5 ,C= 96417 ,D= 1131909510 ,OPMODE= 11_1_11010 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 235088 ,B= 5 ,C= 96417 ,D= 1131909510 ,OPMODE= 11_1_11010 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 162635 ,B= 5 ,C= 95429 ,D= 281474104407192 ,OPMODE= 00_1_10101 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 162635 ,B= 5 ,C= 95429 ,D= 281474104407192 ,OPMODE= 00_1_10101 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 167073 ,B= 5 ,C= 229544 ,D= 1419705769 ,OPMODE= 11_1_01100 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 167073 ,B= 5 ,C= 229544 ,D= 1419705769 ,OPMODE= 11_1_01100 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 130974 ,B= 5 ,C= 138538 ,D= 281474015556749 ,OPMODE= 11_1_00110 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 130974 ,B= 5 ,C= 138538 ,D= 281474015556749 ,OPMODE= 11_1_00110 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 0 ,A= 241351 ,B= 5 ,C= 213267 ,D= 899729771 ,OPMODE= 01_1_11001 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
# CLK= 1 ,A= 241351 ,B= 5 ,C= 213267 ,D= 899729771 ,OPMODE= 01_1_11001 BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
```

- Testing **bypassing the pre-adder**, by forcing A = 1 & C = 0, so the output “P” will take the value of “B” after 4 clock cycle (# Pipeline Stages)
- **Note:**
 - The orange signal are the internal signals of the DUT




```
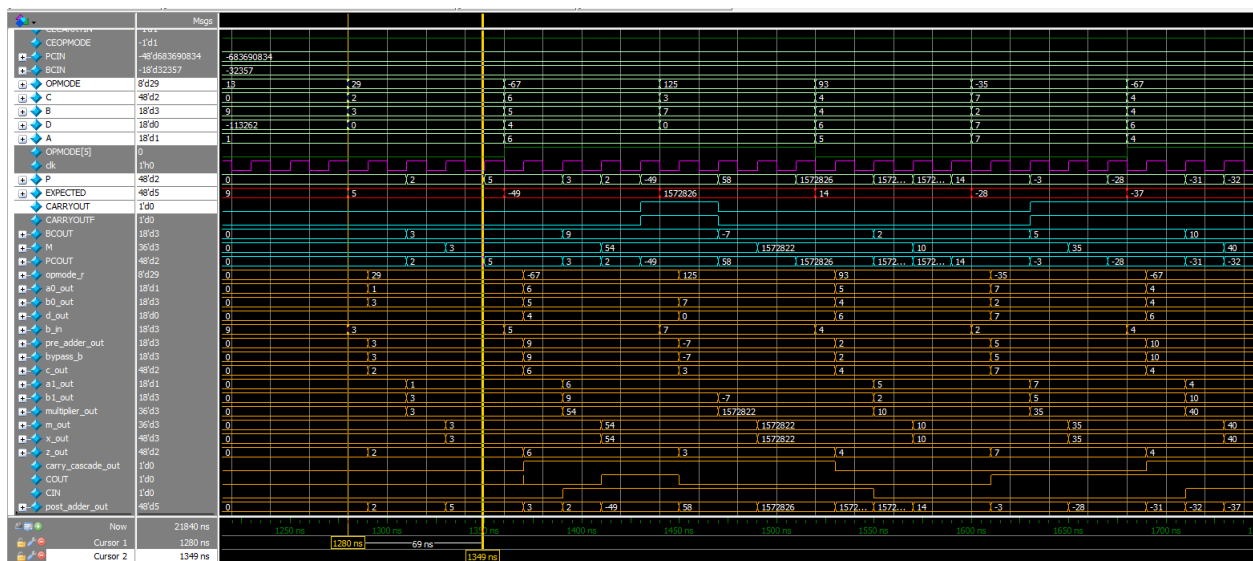
#
# -----> Testing bypass B <-----
#
# CLK= 0 ,D= 175044 ,B= 7 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 7
# CLK= 1 ,D= 175044 ,B= 7 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 7
# CLK= 0 ,D= 175044 ,B= 7 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 7
# CLK= 1 ,D= 175044 ,B= 7 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 7 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 7
# CLK= 0 ,D= 175044 ,B= 7 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 7 ,M= 7 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 7
# CLK= 1 ,D= 175044 ,B= 7 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 7 ,M= 7 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 7
# CLK= 0 ,D= 175044 ,B= 7 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 7 ,M= 7 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 7
# CLK= 1 ,D= 175044 ,B= 7 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 7 ,M= 7 ,CARRYOUT= 0 ,P= 7 ,EXPECTED = 12
# CLK= 0 ,D= 170676 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 7 ,M= 7 ,CARRYOUT= 0 ,P= 7 ,EXPECTED = 12
# CLK= 1 ,D= 170676 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 7 ,M= 7 ,CARRYOUT= 0 ,P= 7 ,EXPECTED = 12
# CLK= 0 ,D= 170676 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 7 ,CARRYOUT= 0 ,P= 7 ,EXPECTED = 12
# CLK= 1 ,D= 170676 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 7 ,CARRYOUT= 0 ,P= 7 ,EXPECTED = 12
# CLK= 0 ,D= 170676 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 7 ,EXPECTED = 12
# CLK= 1 ,D= 170676 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 7 ,EXPECTED = 12
# CLK= 0 ,D= 128506 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
# CLK= 1 ,D= 128506 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
# CLK= 0 ,D= 128506 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
# CLK= 1 ,D= 128506 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
# CLK= 0 ,D= 128506 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
# CLK= 1 ,D= 128506 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
# CLK= 0 ,D= 155325 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
# CLK= 1 ,D= 155325 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
# CLK= 0 ,D= 155325 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
# CLK= 1 ,D= 155325 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
# CLK= 0 ,D= 155325 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
# CLK= 1 ,D= 155325 ,B= 12 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
# CLK= 0 ,D= 249802 ,B= 8 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 8
# CLK= 1 ,D= 249802 ,B= 8 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 12 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 8
# CLK= 0 ,D= 249802 ,B= 8 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 8 ,M= 12 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 8
# CLK= 1 ,D= 249802 ,B= 8 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 8 ,M= 8 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 8
# CLK= 0 ,D= 249802 ,B= 8 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 8 ,M= 8 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 8
# CLK= 1 ,D= 249802 ,B= 8 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 8 ,M= 8 ,CARRYOUT= 0 ,P= 8 ,EXPECTED = 8
# CLK= 0 ,D= 108942 ,B= 7 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 8 ,M= 8 ,CARRYOUT= 0 ,P= 8 ,EXPECTED = 7
# CLK= 1 ,D= 108942 ,B= 7 ,A= 1 ,C= 0 ,OPMODE= 00_0_01101 ,BCOUT= 8 ,M= 8 ,CARRYOUT= 0 ,P= 8 ,EXPECTED = 7


```

- ```
case (OPMODE[7:6])
 2'b00 : begin PRE_EXP = D+B; EXPECTED = C + (A*PRE_EXP + OPMODE[5]); end
 2'b01 : begin PRE_EXP = D-B; EXPECTED = C + (A*PRE_EXP + OPMODE[5]); end
 2'b10 : begin PRE_EXP = D+B; EXPECTED = C - (A*PRE_EXP + OPMODE[5]); end
 2'b11 : begin PRE_EXP = D-B; EXPECTED = C - (A*PRE_EXP + OPMODE[5]); end
endcase
```



| --> Testing arithmetic operations <--> |   |    |        |      |   |    |   |    |   |         |            |        |   |    |    |           |   |    |                 |            |                 |
|----------------------------------------|---|----|--------|------|---|----|---|----|---|---------|------------|--------|---|----|----|-----------|---|----|-----------------|------------|-----------------|
| CLK=                                   | 0 | D= | 148882 | B=   | 9 | A= | 1 | C= | 0 | OPMODE= | 00_0_01101 | BCOUT= | 9 | M= | 9  | CARRYOUT= | 0 | P= | 9               | EXPECTED = | 9               |
| CLK=                                   | 1 | D= | 148882 | B=   | 9 | A= | 1 | C= | 0 | OPMODE= | 00_0_01101 | BCOUT= | 0 | M= | 0  | CARRYOUT= | 0 | P= | 0               | EXPECTED = | 9               |
| CLK=                                   | 0 | D= | 148882 | B=   | 9 | A= | 1 | C= | 0 | OPMODE= | 00_0_01101 | BCOUT= | 0 | M= | 0  | CARRYOUT= | 0 | P= | 0               | EXPECTED = | 9               |
| CLK=                                   | 1 | D= | 148882 | B=   | 9 | A= | 1 | C= | 0 | OPMODE= | 00_0_01101 | BCOUT= | 0 | M= | 0  | CARRYOUT= | 0 | P= | 0               | EXPECTED = | 9               |
| CLK=                                   | 0 | D= | 148882 | B=   | 9 | A= | 1 | C= | 0 | OPMODE= | 00_0_01101 | BCOUT= | 0 | M= | 0  | CARRYOUT= | 0 | P= | 0               | EXPECTED = | 9               |
| CLK=                                   | 1 | D= | 148882 | B=   | 9 | A= | 1 | C= | 0 | OPMODE= | 00_0_01101 | BCOUT= | 0 | M= | 0  | CARRYOUT= | 0 | P= | 0               | EXPECTED = | 9               |
| CLK=                                   | 0 | D= | 148882 | B=   | 9 | A= | 1 | C= | 0 | OPMODE= | 00_0_01101 | BCOUT= | 0 | M= | 0  | CARRYOUT= | 0 | P= | 0               | EXPECTED = | 9               |
| CLK=                                   | 1 | D= | 148882 | B=   | 9 | A= | 1 | C= | 0 | OPMODE= | 00_0_01101 | BCOUT= | 0 | M= | 0  | CARRYOUT= | 0 | P= | 0               | EXPECTED = | 9               |
| CLK=                                   | 0 | D= | 0      | B=   | 3 | A= | 1 | C= | 2 | OPMODE= | 00_0_11101 | BCOUT= | 0 | M= | 0  | CARRYOUT= | 0 | P= | 0               | EXPECTED = | 5               |
| CLK=                                   | 1 | D= | 0      | B=   | 3 | A= | 1 | C= | 2 | OPMODE= | 00_0_11101 | BCOUT= | 0 | M= | 0  | CARRYOUT= | 0 | P= | 0               | EXPECTED = | 5               |
| CLK=                                   | 0 | D= | 0      | B=   | 3 | A= | 1 | C= | 2 | OPMODE= | 00_0_11101 | BCOUT= | 0 | M= | 0  | CARRYOUT= | 0 | P= | 0               | EXPECTED = | 5               |
| CLK=                                   | 1 | D= | 0      | B=   | 3 | A= | 1 | C= | 2 | OPMODE= | 00_0_11101 | BCOUT= | 3 | M= | 3  | CARRYOUT= | 0 | P= | 2               | EXPECTED = | 5               |
| CLK=                                   | 0 | D= | 0      | B=   | 3 | A= | 1 | C= | 2 | OPMODE= | 00_0_11101 | BCOUT= | 3 | M= | 3  | CARRYOUT= | 0 | P= | 2               | EXPECTED = | 5               |
| CLK=                                   | 1 | D= | 0      | B=   | 3 | A= | 1 | C= | 2 | OPMODE= | 00_0_11101 | BCOUT= | 3 | M= | 3  | CARRYOUT= | 0 | P= | 2               | EXPECTED = | 5               |
| CLK=                                   | 0 | D= | 0      | B=   | 3 | A= | 1 | C= | 2 | OPMODE= | 00_0_11101 | BCOUT= | 3 | M= | 3  | CARRYOUT= | 0 | P= | 2               | EXPECTED = | 5               |
| CLK=                                   | 1 | D= | 0      | B=   | 3 | A= | 1 | C= | 2 | OPMODE= | 00_0_11101 | BCOUT= | 3 | M= | 3  | CARRYOUT= | 0 | P= | 2               | EXPECTED = | 5               |
| CLK=                                   | 0 | D= | 0      | B=   | 3 | A= | 1 | C= | 2 | OPMODE= | 00_0_11101 | BCOUT= | 3 | M= | 3  | CARRYOUT= | 0 | P= | 2               | EXPECTED = | 5               |
| CLK=                                   | 1 | D= | 4      | B=   | 5 | A= | 6 | C= | 6 | OPMODE= | 10_1_11101 | BCOUT= | 3 | M= | 3  | CARRYOUT= | 0 | P= | 5               | EXPECTED = | 281474976710607 |
| CLK=                                   | 0 | D= | 4      | B=   | 5 | A= | 6 | C= | 6 | OPMODE= | 10_1_11101 | BCOUT= | 3 | M= | 3  | CARRYOUT= | 0 | P= | 5               | EXPECTED = | 281474976710607 |
| CLK=                                   | 1 | D= | 4      | B=   | 5 | A= | 6 | C= | 6 | OPMODE= | 10_1_11101 | BCOUT= | 3 | M= | 3  | CARRYOUT= | 0 | P= | 5               | EXPECTED = | 281474976710607 |
| CLK=                                   | 0 | D= | 4      | B=   | 5 | A= | 6 | C= | 6 | OPMODE= | 10_1_11101 | BCOUT= | 9 | M= | 9  | CARRYOUT= | 0 | P= | 3               | EXPECTED = | 281474976710607 |
| CLK=                                   | 1 | D= | 4      | B=   | 5 | A= | 6 | C= | 6 | OPMODE= | 10_1_11101 | BCOUT= | 9 | M= | 9  | CARRYOUT= | 0 | P= | 3               | EXPECTED = | 281474976710607 |
| CLK=                                   | 0 | D= | 4      | B=   | 5 | A= | 6 | C= | 6 | OPMODE= | 10_1_11101 | BCOUT= | 9 | M= | 54 | CARRYOUT= | 0 | P= | 2               | EXPECTED = | 281474976710607 |
| CLK=                                   | 1 | D= | 4      | B=   | 5 | A= | 6 | C= | 6 | OPMODE= | 10_1_11101 | BCOUT= | 9 | M= | 54 | CARRYOUT= | 0 | P= | 2               | EXPECTED = | 281474976710607 |
| CLK=                                   | 0 | D= | 4      | B=   | 5 | A= | 6 | C= | 6 | OPMODE= | 10_1_11101 | BCOUT= | 9 | M= | 54 | CARRYOUT= | 1 | P= | 281474976710607 | EXPECTED = | 281474976710607 |
| CLK=                                   | 1 | D= | 0      | B=</ |   |    |   |    |   |         |            |        |   |    |    |           |   |    |                 |            |                 |

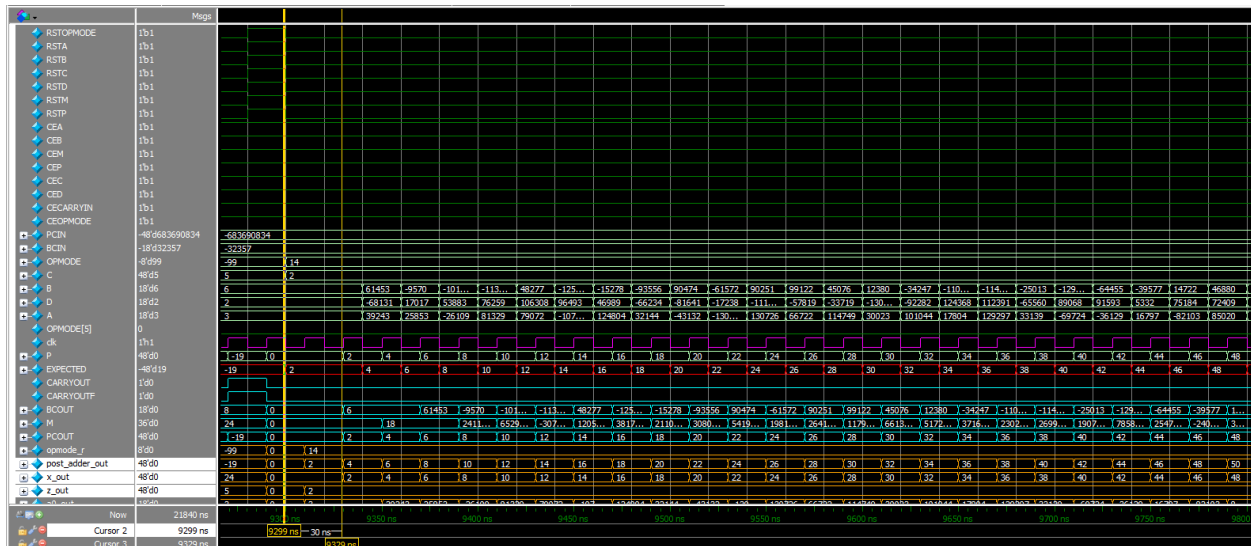- Testing accumulator through Mux "X", the resetting to force all FF's output to be zero, then forcing **C** = 2 to make **P** = 2 after 2 cycles then **P** will be increased by 2 every 1 clock cycle




```

--> Testing Accumulator through X <-----
CLK= 0 ,D= 2 ,B= 6 ,A= 3 ,C= 5 ,OPMODE= 10_0_11101 ,BCOUT= 8 ,M= 24 ,CARRYOUT= 1 ,P= 281474976710637 ,EXPECTED = 281474976710637
CLK= 1 ,D= 2 ,B= 6 ,A= 3 ,C= 5 ,OPMODE= 10_0_11101 ,BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 281474976710637
CLK= 0 ,D= 2 ,B= 6 ,A= 3 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 2 ,B= 6 ,A= 3 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 2 ,B= 6 ,A= 3 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 2 ,B= 6 ,A= 3 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 6 ,M= 0 ,CARRYOUT= 0 ,P= 2 ,EXPECTED = 2
CLK= 0 ,D= 194013 ,B= 61453 ,A= 39243 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 6 ,M= 0 ,CARRYOUT= 0 ,P= 2 ,EXPECTED = 4
CLK= 1 ,D= 194013 ,B= 61453 ,A= 39243 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 6 ,M= 18 ,CARRYOUT= 0 ,P= 4 ,EXPECTED = 4
CLK= 0 ,D= 17017 ,B= 252574 ,A= 25853 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 6 ,M= 18 ,CARRYOUT= 0 ,P= 4 ,EXPECTED = 6
CLK= 1 ,D= 17017 ,B= 252574 ,A= 25853 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 61453 ,M= 18 ,CARRYOUT= 0 ,P= 6 ,EXPECTED = 6
CLK= 0 ,D= 53883 ,B= 160655 ,A= 236035 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 61453 ,M= 18 ,CARRYOUT= 0 ,P= 6 ,EXPECTED = 8
CLK= 1 ,D= 53883 ,B= 160655 ,A= 236035 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 252574 ,M= 2411600079 ,CARRYOUT= 0 ,P= 8 ,EXPECTED = 8
CLK= 0 ,D= 76259 ,B= 148253 ,A= 81329 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 252574 ,M= 2411600079 ,CARRYOUT= 0 ,P= 8 ,EXPECTED = 10
CLK= 1 ,D= 76259 ,B= 148253 ,A= 81329 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 160655 ,M= 6529795622 ,CARRYOUT= 0 ,P= 10 ,EXPECTED = 10
CLK= 0 ,D= 106308 ,B= 48277 ,A= 79072 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 160655 ,M= 6529795622 ,CARRYOUT= 0 ,P= 10 ,EXPECTED = 12
CLK= 1 ,D= 106308 ,B= 48277 ,A= 79072 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 148253 ,M= 37920202925 ,CARRYOUT= 0 ,P= 12 ,EXPECTED = 12
CLK= 0 ,D= 96493 ,B= 136530 ,A= 154616 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 148253 ,M= 37920202925 ,CARRYOUT= 0 ,P= 14 ,EXPECTED = 14
CLK= 1 ,D= 96493 ,B= 136530 ,A= 154616 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 48277 ,M= 12057268237 ,CARRYOUT= 0 ,P= 14 ,EXPECTED = 16
CLK= 0 ,D= 46989 ,B= 246866 ,A= 124804 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 48277 ,M= 12057268237 ,CARRYOUT= 0 ,P= 14 ,EXPECTED = 16
CLK= 1 ,D= 46989 ,B= 246866 ,A= 124804 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 136530 ,M= 3817358944 ,CARRYOUT= 0 ,P= 16 ,EXPECTED = 16
CLK= 0 ,D= 195910 ,B= 168588 ,A= 32144 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 136530 ,M= 3817358944 ,CARRYOUT= 0 ,P= 16 ,EXPECTED = 18
CLK= 1 ,D= 195910 ,B= 168588 ,A= 32144 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 246866 ,M= 21109722480 ,CARRYOUT= 0 ,P= 18 ,EXPECTED = 18
CLK= 0 ,D= 180503 ,B= 90474 ,A= 219012 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 246866 ,M= 21109722480 ,CARRYOUT= 0 ,P= 18 ,EXPECTED = 20
CLK= 1 ,D= 180503 ,B= 90474 ,A= 219012 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 168588 ,M= 30809864264 ,CARRYOUT= 0 ,P= 20 ,EXPECTED = 20
CLK= 0 ,D= 244906 ,B= 200572 ,A= 131680 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 168588 ,M= 30809864264 ,CARRYOUT= 0 ,P= 20 ,EXPECTED = 22
CLK= 1 ,D= 244906 ,B= 200572 ,A= 131680 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 90474 ,M= 5419092672 ,CARRYOUT= 0 ,P= 22 ,EXPECTED = 22
CLK= 0 ,D= 150970 ,B= 90251 ,A= 130726 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 90474 ,M= 5419092672 ,CARRYOUT= 0 ,P= 22 ,EXPECTED = 24
CLK= 1 ,D= 150970 ,B= 90251 ,A= 130726 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 200572 ,M= 19814891688 ,CARRYOUT= 0 ,P= 24 ,EXPECTED = 24
CLK= 0 ,D= 204325 ,B= 99122 ,A= 66722 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 200572 ,M= 19814891688 ,CARRYOUT= 0 ,P= 24 ,EXPECTED = 26
CLK= 1 ,D= 204325 ,B= 99122 ,A= 66722 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 90251 ,M= 26411320960 ,CARRYOUT= 0 ,P= 26 ,EXPECTED = 26
CLK= 0 ,D= 228425 ,B= 45076 ,A= 114749 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 90251 ,M= 26411320960 ,CARRYOUT= 0 ,P= 26 ,EXPECTED = 28
CLK= 1 ,D= 228425 ,B= 45076 ,A= 114749 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 90251 ,M= 11208152926 ,CARRYOUT= 0 ,P= 28 ,EXPECTED = 28

```



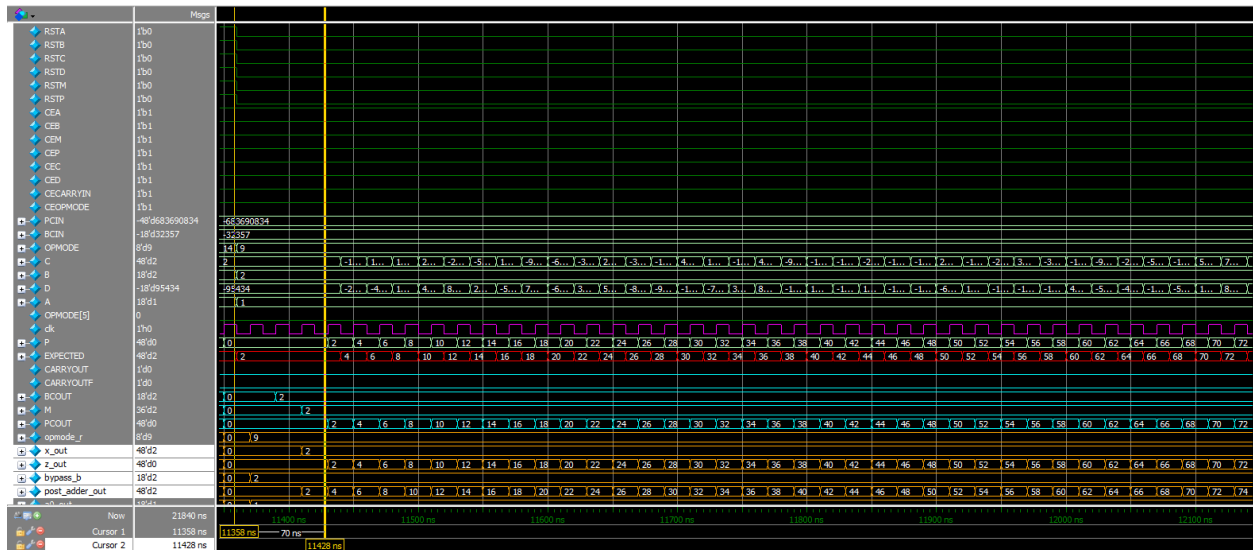- Testing accumulator through Mux "Z", the resetting to force all FF's output to be zero, then bypassing **B** = 2, then mutiply it by **A** = 1 to make **P** = 2 after 4 cycles then **P** will be increased by 2 every 1 clock cycle




```

-----> Testing Accumulator through Z <-----
CLK= 0 ,D= 166710 ,B= 131890 ,A= 206969 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 16900 ,M= 39697527936 ,CARRYOUT= 0 ,P= 202 ,EXPECTED = 202
CLK= 1 ,D= 166710 ,B= 131890 ,A= 206969 ,C= 2 ,OPMODE= 00_0_01110 ,BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 202
CLK= 0 ,D= 166710 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 166710 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 166710 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 0 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 166710 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 0 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 166710 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 166710 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 166710 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 166710 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 241380 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 241380 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 241380 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 241380 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 257194 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 257194 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 100398 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 100398 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 49777 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 49777 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 8636 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 8636 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 22295 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 22295 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 205291 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 205291 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 77449 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 77449 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 194239 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 194239 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 194239 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 194239 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 39635 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 39635 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 52354 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 52354 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 173937 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 173937 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 0 ,D= 167438 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2
CLK= 1 ,D= 167438 ,B= 2 ,A= 1 ,C= 2 ,OPMODE= 00_0_01001 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 2

```



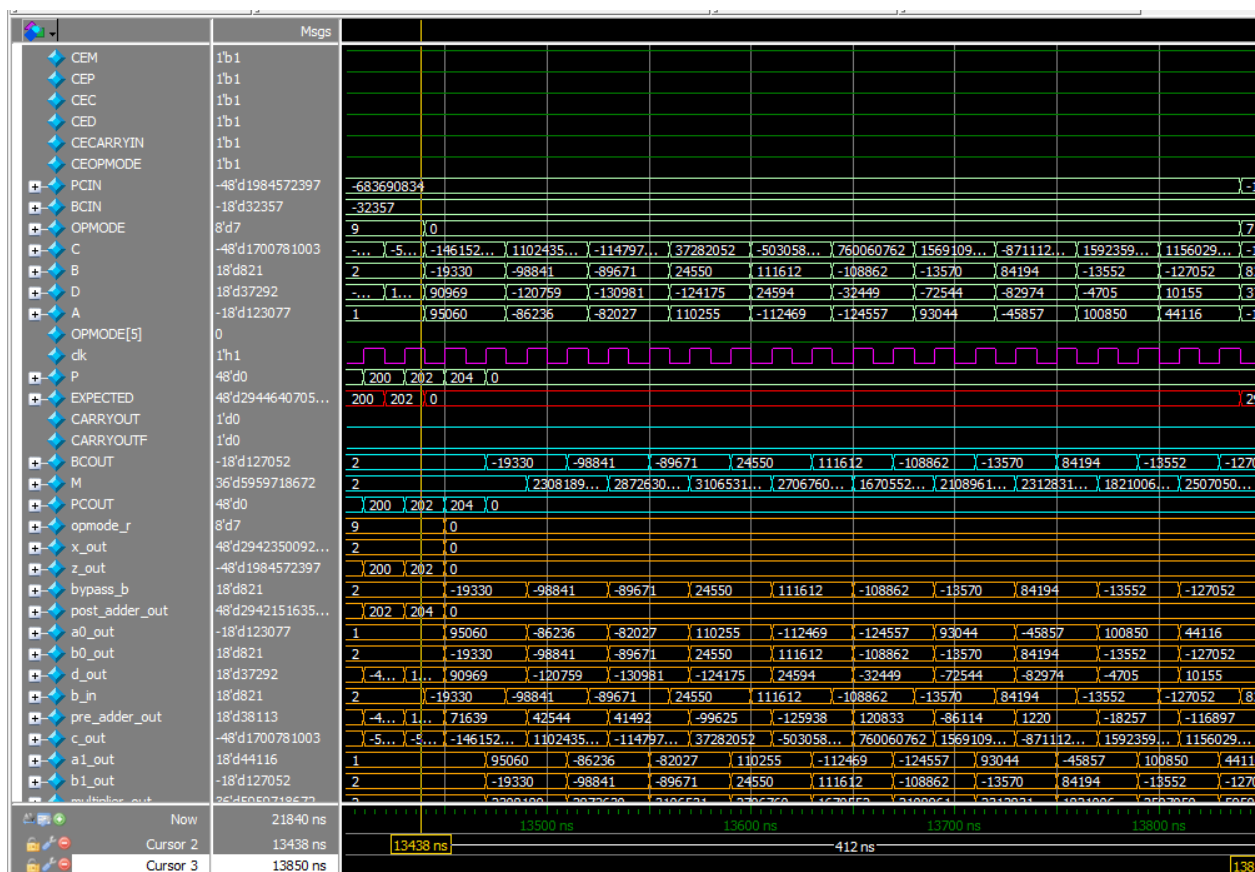- Testing Placing all zeros in the two Muxs (Mux X & Mux Z)




```
 
#-----> Testing Placing all zeros <-----
#
CLK= 0 ,D= 4216 ,B= 3367 ,A= 75359 ,C= 297818915 ,OPMODE= 00_0_00000 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 202 ,EXPECTED = 0
CLK= 1 ,D= 4216 ,B= 3367 ,A= 75359 ,C= 297818915 ,OPMODE= 00_0_00000 ,BCOUT= 2 ,M= 2 ,CARRYOUT= 0 ,P= 204 ,EXPECTED = 0
CLK= 0 ,D= 4216 ,B= 3367 ,A= 75359 ,C= 297818915 ,OPMODE= 00_0_00000 ,BCOUT= 3367 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 0 ,D= 191403 ,B= 137016 ,A= 216354 ,C= 1693629897 ,OPMODE= 00_0_00000 ,BCOUT= 3367 ,M= 2 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 1 ,D= 191403 ,B= 137016 ,A= 216354 ,C= 1693629897 ,OPMODE= 00_0_00000 ,BCOUT= 3367 ,M= 253733753 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 0 ,D= 191403 ,B= 137016 ,A= 216354 ,C= 1693629897 ,OPMODE= 00_0_00000 ,BCOUT= 3367 ,M= 253733753 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 1 ,D= 191403 ,B= 137016 ,A= 216354 ,C= 1693629897 ,OPMODE= 00_0_00000 ,BCOUT= 137016 ,M= 253733753 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 0 ,D= 216263 ,B= 25218 ,A= 55246 ,C= 281474499486407 ,OPMODE= 00_0_00000 ,BCOUT= 137016 ,M= 29643959664 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 1 ,D= 216263 ,B= 25218 ,A= 55246 ,C= 281474499486407 ,OPMODE= 00_0_00000 ,BCOUT= 137016 ,M= 29643959664 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 0 ,D= 216263 ,B= 25218 ,A= 55246 ,C= 281474499486407 ,OPMODE= 00_0_00000 ,BCOUT= 137016 ,M= 29643959664 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 1 ,D= 216263 ,B= 25218 ,A= 55246 ,C= 281474499486407 ,OPMODE= 00_0_00000 ,BCOUT= 25218 ,M= 29643959664 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 0 ,D= 238628 ,B= 225243 ,A= 70664 ,C= 985821045 ,OPMODE= 00_0_00000 ,BCOUT= 25218 ,M= 1393193628 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 1 ,D= 238628 ,B= 225243 ,A= 70664 ,C= 985821045 ,OPMODE= 00_0_00000 ,BCOUT= 25218 ,M= 1393193628 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 0 ,D= 238628 ,B= 225243 ,A= 70664 ,C= 985821045 ,OPMODE= 00_0_00000 ,BCOUT= 25218 ,M= 1393193628 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 1 ,D= 238628 ,B= 225243 ,A= 70664 ,C= 985821045 ,OPMODE= 00_0_00000 ,BCOUT= 225243 ,M= 1393193628 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 0 ,D= 204213 ,B= 94746 ,A= 135992 ,C= 281473922054786 ,OPMODE= 00_0_00000 ,BCOUT= 225243 ,M= 15916571352 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 1 ,D= 204213 ,B= 94746 ,A= 135992 ,C= 281473922054786 ,OPMODE= 00_0_00000 ,BCOUT= 225243 ,M= 15916571352 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 0 ,D= 204213 ,B= 94746 ,A= 135992 ,C= 281473922054786 ,OPMODE= 00_0_00000 ,BCOUT= 94746 ,M= 15916571352 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 1 ,D= 204213 ,B= 94746 ,A= 135992 ,C= 281473922054786 ,OPMODE= 00_0_00000 ,BCOUT= 94746 ,M= 12884698032 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 0 ,D= 106584 ,B= 158288 ,A= 39587 ,C= 1380180900 ,OPMODE= 00_0_00000 ,BCOUT= 94746 ,M= 15916571352 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 1 ,D= 106584 ,B= 158288 ,A= 39587 ,C= 1380180900 ,OPMODE= 00_0_00000 ,BCOUT= 94746 ,M= 12884698032 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 0 ,D= 106584 ,B= 158288 ,A= 39587 ,C= 1380180900 ,OPMODE= 00_0_00000 ,BCOUT= 94746 ,M= 12884698032 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 1 ,D= 106584 ,B= 158288 ,A= 39587 ,C= 1380180900 ,OPMODE= 00_0_00000 ,BCOUT= 158288 ,M= 12884698032 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 0 ,D= 253797 ,B= 6122 ,A= 14598 ,C= 281473535148116 ,OPMODE= 00_0_00000 ,BCOUT= 158288 ,M= 12884698032 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0
CLK= 1 ,D= 253797 ,B= 6122 ,A= 14598 ,C= 281473535148116 ,OPMODE= 00_0_00000 ,BCOUT= 158288 ,M= 6266147056 ,CARRYOUT= 0 ,P= 0 ,EXPECTED = 0

```

- Testing Concatenation & PCIN, the (correct concatenated output+ PCIN) will be available after 3 clock cycle after forcing the inputs (**A,B,C,D** and **OPMODE**)
- **Note:**  
There is no relation between concatenation & PCIN, I just have tested them together as they are simple cases. However, PCIN can be used with the other functionalities.



```
CLK= 0 ,D= 94108 ,B= 222998 ,A= 230432 ,C= 281474459889346 ,OPMODE= 00_0_00111 ,BCOUT= 98085 ,M= 5798294775 ,CARRYOUT= 1 ,P= 90243379841990 ,EXPECTED = 274661678458180
CLK= 1 ,D= 94108 ,B= 222998 ,A= 230432 ,C= 281474459889346 ,OPMODE= 00_0_00111 ,BCOUT= 98085 ,M= 5798294775 ,CARRYOUT= 1 ,P= 90242412526931 ,EXPECTED = 274661678458180
CLK= 0 ,D= 94108 ,B= 222998 ,A= 230432 ,C= 281474459889346 ,OPMODE= 00_0_00111 ,BCOUT= 98085 ,M= 5798294775 ,CARRYOUT= 1 ,P= 90242412526931 ,EXPECTED = 274661678458180
CLK= 1 ,D= 94108 ,B= 222998 ,A= 230432 ,C= 281474459889346 ,OPMODE= 00_0_00111 ,BCOUT= 222998 ,M= 5798294775 ,CARRYOUT= 1 ,P= 274616768609619 ,EXPECTED = 274661678458180
CLK= 0 ,D= 94108 ,B= 222998 ,A= 230432 ,C= 281474459889346 ,OPMODE= 00_0_00111 ,BCOUT= 222998 ,M= 5798294775 ,CARRYOUT= 1 ,P= 274616768609619 ,EXPECTED = 274661678458180
CLK= 1 ,D= 94108 ,B= 222998 ,A= 230432 ,C= 281474459889346 ,OPMODE= 00_0_00111 ,BCOUT= 222998 ,M= 51385875136 ,CARRYOUT= 1 ,P= 274661678458180 ,EXPECTED = 274661678458180
CLK= 0 ,D= 94108 ,B= 222998 ,A= 230432 ,C= 281474459889346 ,OPMODE= 00_0_00111 ,BCOUT= 222998 ,M= 51385875136 ,CARRYOUT= 1 ,P= 274661678458180 ,EXPECTED = 274661678458180
CLK= 1 ,D= 94108 ,B= 222998 ,A= 230432 ,C= 281474459889346 ,OPMODE= 00_0_00111 ,BCOUT= 222998 ,M= 51385875136 ,CARRYOUT= 1 ,P= 274661678458180 ,EXPECTED = 274661678458180
CLK= 0 ,D= 10797 ,B= 186629 ,A= 106503 ,C= 1952183784 ,OPMODE= 00_0_00111 ,BCOUT= 222998 ,M= 51385875136 ,CARRYOUT= 1 ,P= 274661678458180 ,EXPECTED = 179041259803034
CLK= 1 ,D= 10797 ,B= 186629 ,A= 106503 ,C= 1952183784 ,OPMODE= 00_0_00111 ,BCOUT= 222998 ,M= 51385875136 ,CARRYOUT= 1 ,P= 274662539222955 ,EXPECTED = 179041259803034
CLK= 0 ,D= 10797 ,B= 186629 ,A= 106503 ,C= 1952183784 ,OPMODE= 00_0_00111 ,BCOUT= 222998 ,M= 51385875136 ,CARRYOUT= 1 ,P= 274662539222955 ,EXPECTED = 179041259803034
CLK= 1 ,D= 10797 ,B= 186629 ,A= 106503 ,C= 1952183784 ,OPMODE= 00_0_00111 ,BCOUT= 186629 ,M= 51385875136 ,CARRYOUT= 1 ,P= 179073747083179 ,EXPECTED = 179041259803034
CLK= 0 ,D= 10797 ,B= 186629 ,A= 106503 ,C= 1952183784 ,OPMODE= 00_0_00111 ,BCOUT= 186629 ,M= 19876548387 ,CARRYOUT= 1 ,P= 179041259803034 ,EXPECTED = 179041259803034
CLK= 1 ,D= 10797 ,B= 186629 ,A= 106503 ,C= 1952183784 ,OPMODE= 00_0_00111 ,BCOUT= 186629 ,M= 19876548387 ,CARRYOUT= 1 ,P= 179041259803034 ,EXPECTED = 179041259803034
CLK= 0 ,D= 10797 ,B= 186629 ,A= 106503 ,C= 1952183784 ,OPMODE= 00_0_00111 ,BCOUT= 186629 ,M= 19876548387 ,CARRYOUT= 1 ,P= 179041259803034 ,EXPECTED = 179041259803034
CLK= 1 ,D= 10797 ,B= 186629 ,A= 106503 ,C= 1952183784 ,OPMODE= 00_0_00111 ,BCOUT= 186629 ,M= 19876548387 ,CARRYOUT= 1 ,P= 179041259803034 ,EXPECTED = 179041259803034
---> NO ERRORS, All Outputs are Correct :) <---
** Note: $stop : TB_DSP.v(246)
Time: 21840 ns Iteration: 1 Instance: /TB_DSP
Break in Module TB_DSP at TB_DSP.v line 246
VSI(pause)>
```

## Constraint File

```
Constraints_basys3.xdc
5
6 ## Clock signal
7 set_property -dict { PACKAGE_PIN W5 IOSTANDARD LVCMOS33 } [get_ports CLK]
8 create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports CLK]
9
```

## Elaboration

- Messages tab after elaboration.
- As shown in the snippet → **No critical warnings or errors.**

**Messages**

Warning (22) Info (20) Status (11) Show All


Elaborated Design (22 warnings)

General Messages (22 warnings)

[Synth 8-3331] design REG\_MUX\_\_parameterized0 has unconnected port CLK (21 more like this)

- [Synth 8-3331] design REG\_MUX\_\_parameterized0 has unconnected port RST
- [Synth 8-3331] design REG\_MUX\_\_parameterized0 has unconnected port EN
- [Synth 8-3331] design DSP\_48A1 has unconnected port CARRYIN
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[17]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[16]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[15]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[14]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[13]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[12]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[11]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[10]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[9]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[8]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[7]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[6]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[5]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[4]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[3]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[2]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[1]
- [Synth 8-3331] design DSP\_48A1 has unconnected port BCIN[0]

- Schematic after elaboration.

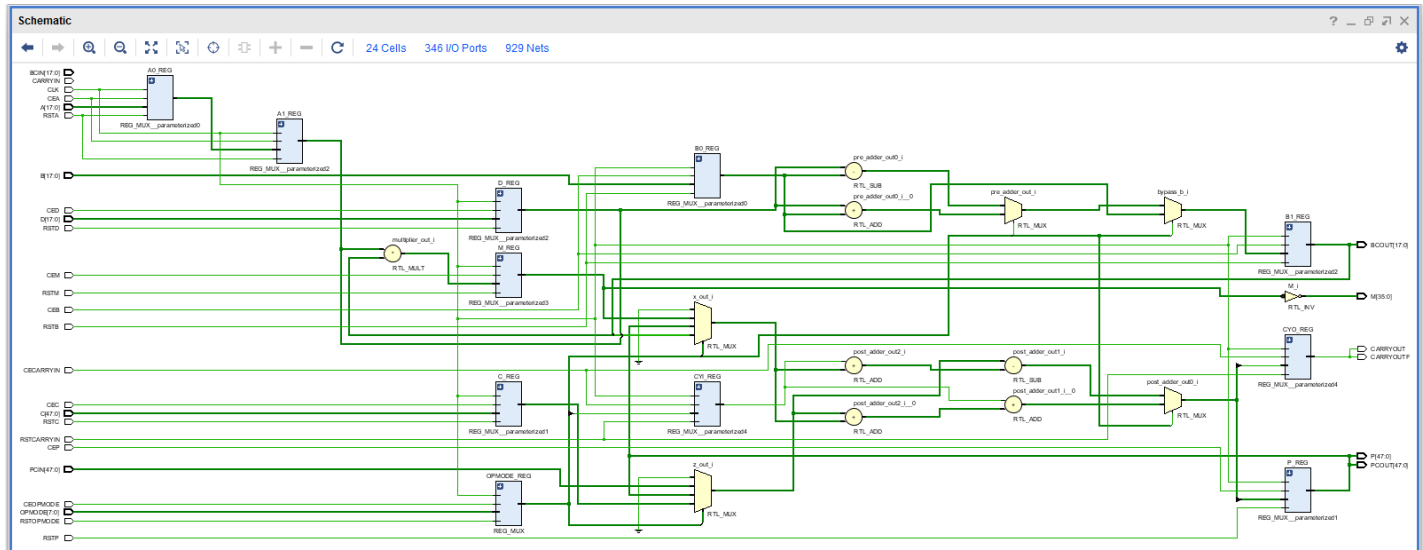

## Synthesis

- Messages tab after running synthesis.
- As shown in the snippet → **No critical warnings or errors.**

Tcl Console Messages x Log Reports Design Runs

☐ Search 
 ☐ Filter 
 ☐ Sort 
 ☒ Show All 
 ☐ Warning (64) 
 ☐ Info (52) 
 ☐ Status (24)

- Elaborated Design (22 warnings)
  - General Messages (22 warnings)
    - [Synth 8-3331] design REG\_MUX\_\_parameterized0 has unconnected port CLK (21 more like this)
- Synthesis (42 warnings)
  - [Synth 8-3331] design REG\_MUX\_\_parameterized0 has unconnected port CLK (40 more like this)
  - [Constraints 18-5210] No constraint will be written out.

- Utilization after running synthesis.

SYNTHESIZED DESIGN - xc7a200tffg1156-3 (active)

Tcl Console Messages Log Reports Design Runs **Utilization** × Debug

◀ Summary ▶

| Resource | Utilization | Available | Utilization % |
|----------|-------------|-----------|---------------|
| LUT      | 230         | 134600    | 0.17          |
| FF       | 160         | 269200    | 0.06          |
| DSP      | 1           | 740       | 0.14          |
| IO       | 327         | 500       | 65.40         |


A horizontal bar chart illustrating the utilization of resources. The x-axis represents Utilization (%) from 0 to 100. The y-axis lists the resources: LUT, FF, DSP, and IO. The bars show that IO is the most utilized resource at 65.40%, while LUT, FF, and DSP are all below 1%.

| Resource | Utilization % |
|----------|---------------|
| LUT      | 0.17          |
| FF       | 0.06          |
| DSP      | 0.14          |
| IO       | 65.40         |


- Timing Summary after running synthesis.
- As shown in the snippet:
  - **Both setup time & hold time slacks are positive.**
  - **Which means that there no timing violations.**

|                                                |          |     |                                  |             |        |                                                   |             |       |
|------------------------------------------------|----------|-----|----------------------------------|-------------|--------|---------------------------------------------------|-------------|-------|
| Tcl Console                                    | Messages | Log | Reports                          | Design Runs | Timing | ×                                                 | Utilization | Debug |
| Design Timing Summary                          |          |     |                                  |             |        |                                                   |             |       |
| Setup                                          |          |     | Hold                             |             |        | Pulse Width                                       |             |       |
| Worst Negative Slack (WNS): 5.168 ns           |          |     | Worst Hold Slack (WHS): 0.182 ns |             |        | Worst Pulse Width Slack (WPWS): 4.500 ns          |             |       |
| Total Negative Slack (TNS): 0.000 ns           |          |     | Total Hold Slack (THS): 0.000 ns |             |        | Total Pulse Width Negative Slack (TPWS): 0.000 ns |             |       |
| Number of Failing Endpoints: 0                 |          |     | Number of Failing Endpoints: 0   |             |        | Number of Failing Endpoints: 0                    |             |       |
| Total Number of Endpoints: 87                  |          |     | Total Number of Endpoints: 87    |             |        | Total Number of Endpoints: 162                    |             |       |
| All user specified timing constraints are met. |          |     |                                  |             |        |                                                   |             |       |
| Timing Summary - timing_1                      |          |     |                                  |             |        |                                                   |             |       |

- Schematic after running synthesis.

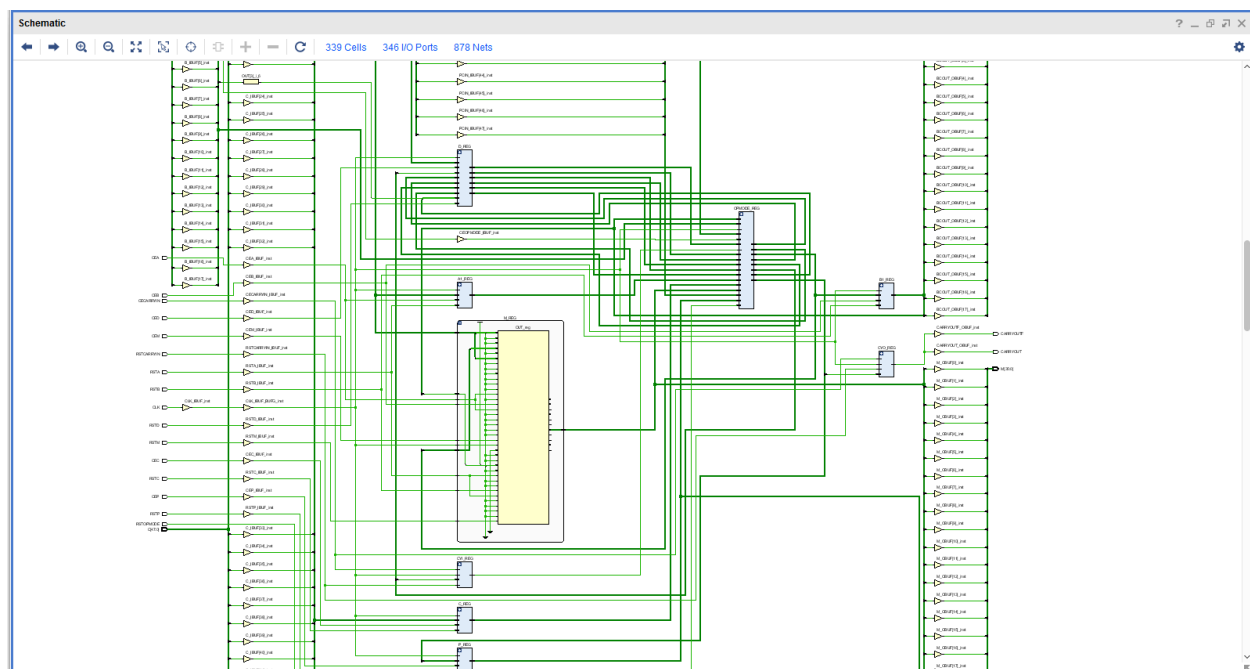

 - Schematic after running synthesis (Zoomed Out).



## Implementation

- Messages tab after running implementation.
- As shown in the snippet → **No critical warnings or errors.**

The screenshot shows the Messages tab in the Vivado IDE. The top bar includes tabs for Tcl Console, Messages, Log, Reports, Design Runs, Power, DRC, Methodology, Timing, and Utilization. Below the tabs, there are icons for search, zoom, and other functions. A summary bar indicates 42 warnings, 225 info messages, and 460 status messages. A 'Show All' button is present. The main area lists the following categories:

- > Vivado Commands (3 infos)
- > Synthesis (42 warnings, 32 infos)
- > Synthesized Design (5 infos)
- > Implementation (88 infos)
- > Implemented Design (9 infos)

- Utilization after implementation.

The screenshot shows the Utilization tab in the Vivado IDE. The top bar includes tabs for Tcl Console, Messages, Log, Reports, Design Runs, Power, DRC, Methodology, Timing, and Utilization. The main area displays a 'Summary' section with a table of resource utilization:

| Resource | Utilization | Available | Utilization % |
|----------|-------------|-----------|---------------|
| LUT      | 229         | 133800    | 0.17          |
| FF       | 179         | 267600    | 0.07          |
| DSP      | 1           | 740       | 0.14          |
| IO       | 327         | 500       | 65.40         |

Below the table is a horizontal bar chart showing the utilization percentage for each resource. The x-axis is labeled 'Utilization (%)' and ranges from 0 to 100. The bars are green, and the values are displayed next to them:

- LUT: 1%
- FF: 1%
- DSP: 1%
- IO: 65%

At the bottom of the Utilization tab, there is a text box labeled 'utilization\_imp'.

- Timing Summary after implementation.
- As shown in the snippet:
  - **Both setup time & hold time slacks are positive.**
  - **Which means that there no timing violations.**

|                                                |          |     |                                  |             |       |                                                   |             |        |   |             |
|------------------------------------------------|----------|-----|----------------------------------|-------------|-------|---------------------------------------------------|-------------|--------|---|-------------|
| Tcl Console                                    | Messages | Log | Reports                          | Design Runs | Power | DRC                                               | Methodology | Timing | x | Utilization |
| Design Timing Summary                          |          |     |                                  |             |       |                                                   |             |        |   |             |
| Setup                                          |          |     | Hold                             |             |       | Pulse Width                                       |             |        |   |             |
| Worst Negative Slack (WNS): 3.612 ns           |          |     | Worst Hold Slack (WHS): 0.273 ns |             |       | Worst Pulse Width Slack (WPWS): 4.500 ns          |             |        |   |             |
| Total Negative Slack (TNS): 0.000 ns           |          |     | Total Hold Slack (THS): 0.000 ns |             |       | Total Pulse Width Negative Slack (TPWS): 0.000 ns |             |        |   |             |
| Number of Failing Endpoints: 0                 |          |     | Number of Failing Endpoints: 0   |             |       | Number of Failing Endpoints: 0                    |             |        |   |             |
| Total Number of Endpoints: 106                 |          |     | Total Number of Endpoints: 106   |             |       | Total Number of Endpoints: 181                    |             |        |   |             |
| All user specified timing constraints are met. |          |     |                                  |             |       |                                                   |             |        |   |             |
| Timing Summary - timing_imp                    |          |     |                                  |             |       |                                                   |             |        |   |             |

- Device snippet.

